

Name : _____

Target grade: _____



Design & Technology Department

GCSE Electronic Products Revision Exercises *Part I*

Topics:

Power Supplies
Voltage Regulators
Thyristors
Astable & Monostable Circuits
Comparators

Mr. Clarvis

Cells


Label each of the cells with the appropriate size name choosing from (C,D,AAA,AA):



Describe the difference between a cell and a battery:

Batteries

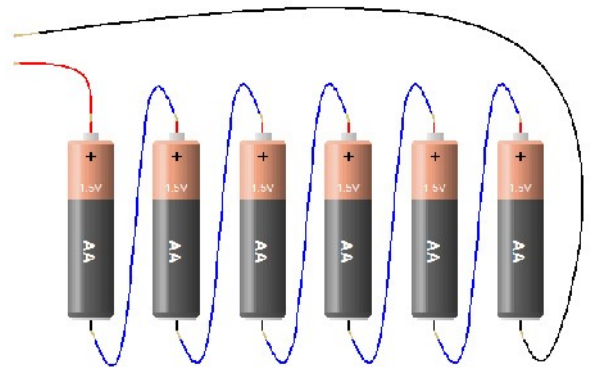Draw the circuit diagram for the circuit shown on the right.



What is the voltage produced by this circuit? _____

Describe three advantages of using rechargeable batteries over conventional batteries:


Describe three advantages and three disadvantages of solar panels:

Draw the circuit symbol for the component shown here:



Circuit no.1: Voltage Regulator

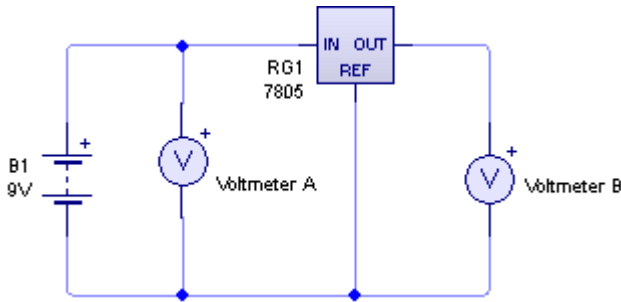Tip: The 7805 can be found under “power supplies” & the voltmeters can be found under “virtual instruments”.



What is the voltage on the input of the voltage regulator?: _____


What is the voltage on the output of the voltage regulator?: _____

Describe what you think the voltage regulator is doing: _____

Describe a situation when you might need this circuit: _____

Circuit no.2: Diodes


Now add a diode to the circuit

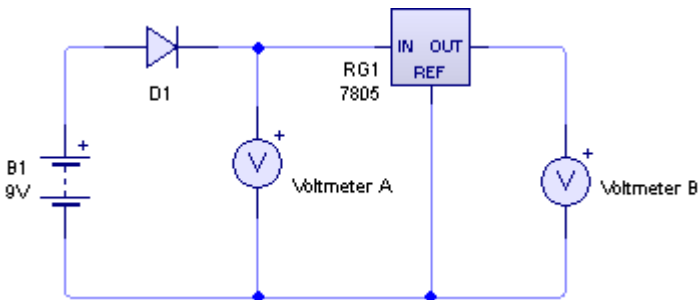

What is the input voltage on the input of the voltage regulator? _____

What is the output voltage on the input of the voltage regulator? _____

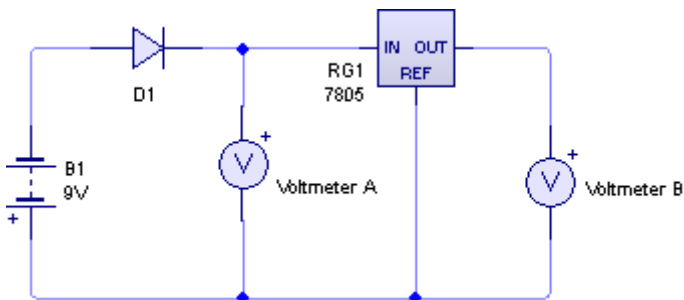Now switch the polarity of the battery round




What is the input voltage on the input of the voltage regulator? _____

What is the output voltage on the input of the voltage regulator? _____

From your experiment above, describe what the diode is doing and why it can be added to any circuit in a similar way:

Circuit no.3: Thyristors

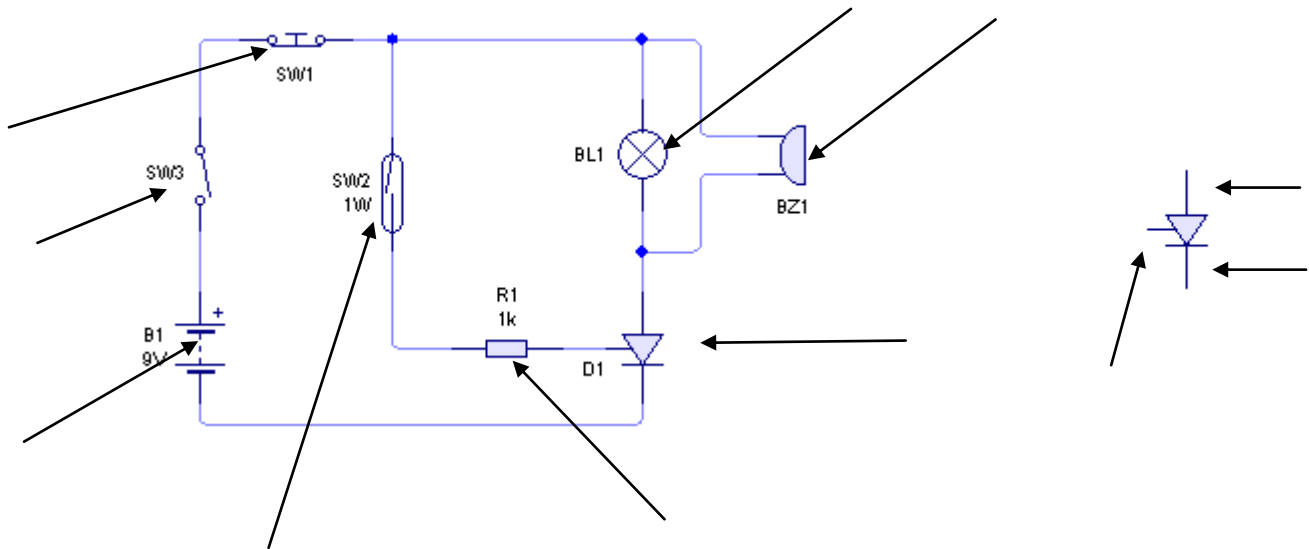Label each of the components on the circuit diagram:



Describe what happens when you first turn on the circuit (by closing switch 3):


Describe what happens when you move a magnet over the reed switch (switch 2):

Describe what happens when you press switch 1:

Describe what action would have a similar effect to pressing switch 1:

Circuit no.4: Astable Circuit

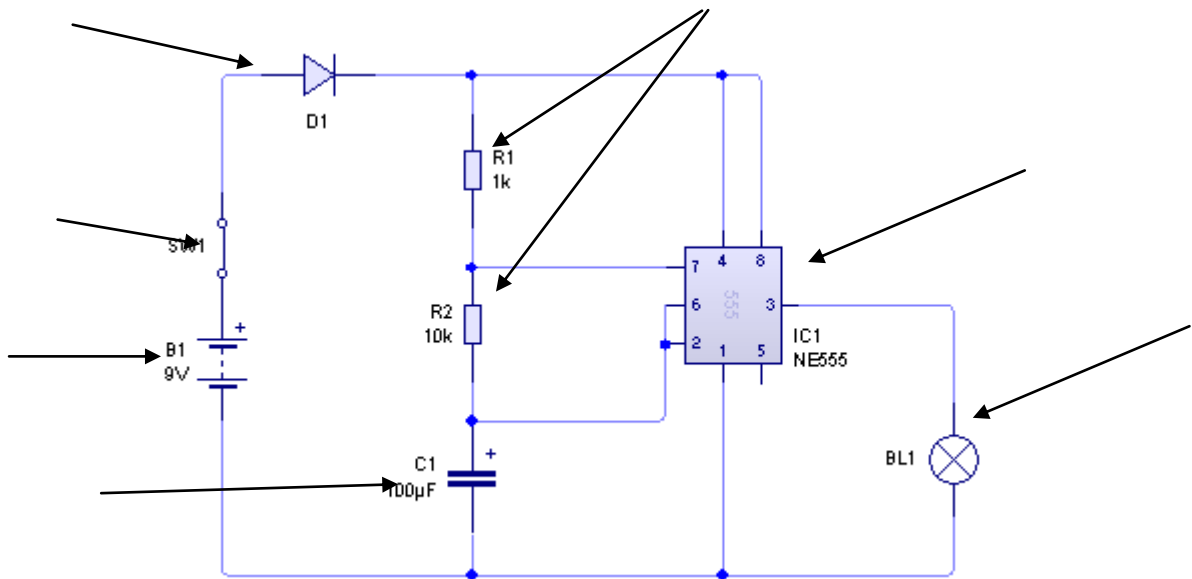Take care to make sure that all of the resistor and capacitor values are set correctly
Label each of the components on the circuit diagram:



Describe why the circuit has the diode included:


Describe what happens when the circuit is switched on:

Change the capacitor value to 200µF, and describe what effect this has on the output. Explain why this happens:

Change the capacitor value to 50µF, and describe what effect this has on the output. Explain why this happens:

Astable Circuits Continued

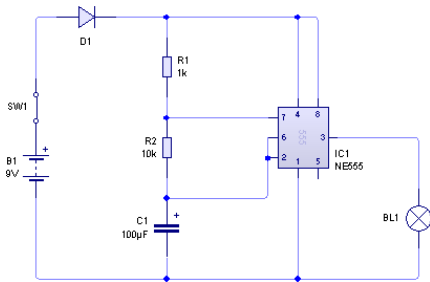For each of the component value sets calculate the output frequency using the formula shown. You will need a scientific calculator. Use the space provided and remember to show your workings.



$$F = \frac{1.44}{(R1 + 2 \times R2) \times C}$$

Question 1

R1 = 1K
R2 = 10K
C1 = 1µF

Question 2

R1 = 100R
R2 = 30R
C1 = 10µF

Question 3

R1 = 100K
R2 = 220K
C1 = 47µF

Question 4

R1 = 47K
R2 = 56K
C1 = 2µF


Question 5

R1 = 12K
R2 = 147K
C1 = 18µF

Circuit no.5: Monostable Circuit

Take care to make sure that all of the resistor and capacitor values are set correctly

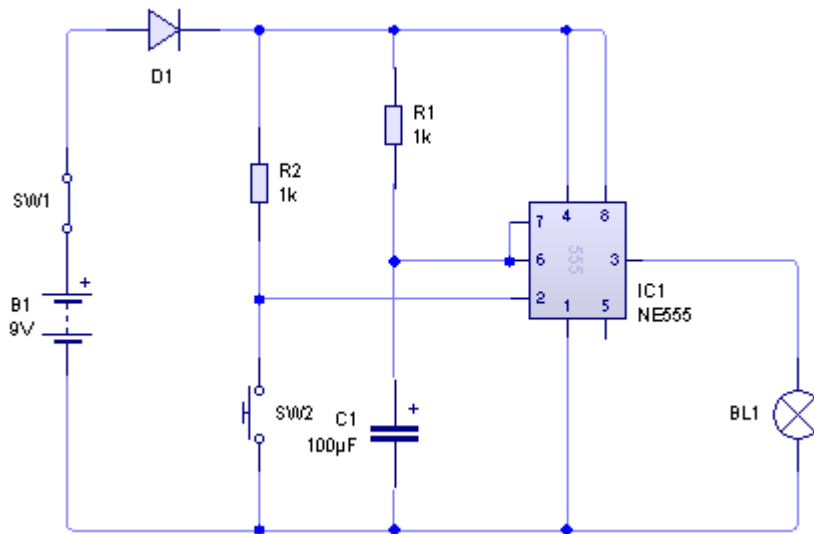Label each of the components on the circuit diagram:



Describe what happens when the circuit is first switched on:

What is the voltage on pin2 when the circuit is first switched on? _____

What is the voltage on pins 6 and 7 when the circuit is first switched on?


What is the voltage on pin2 when the switch 2 is pressed? _____

Describe what happens to the voltage on pins 6 and 7 once switch 2 has been pressed?

Describe what happens to the output once the output has been pressed:

Monostable Circuits Continued

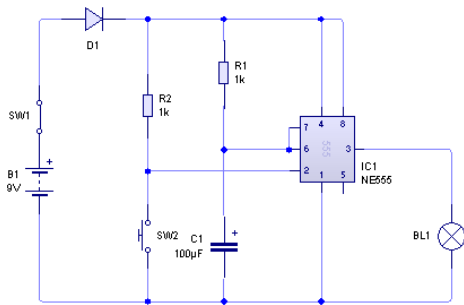For each of the component value sets calculate the time the output is switched on once the circuit has been triggered. Remember to show your workings.



$$T = 1.1 \times R1 \times C1$$

Question 1

$R1 = 1K$
 $C1 = 1\mu F$

Question 2

$R1 = 100R$
 $C1 = 10\mu F$

Question 3

$R1 = 100K$
 $C1 = 47\mu F$

Question 4


$R1 = 47K$
 $C1 = 2\mu F$

Question 5

$R1 = 12K$
 $C1 = 18\mu F$

Circuit no.6: Comparator Circuits

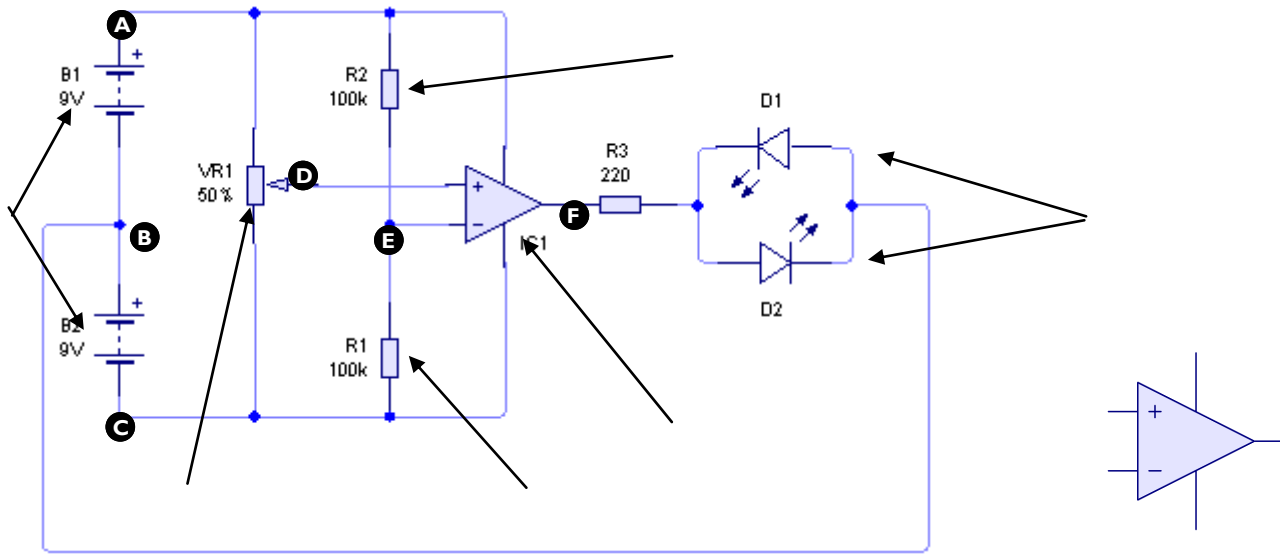Label each of the components on the circuit diagram, build the circuit and complete the tables for the different potentiometer settings.



Set the potentiometer to **0%**

Set the potentiometer to **25%**

Set the potentiometer to **80%**

Test Point	Voltage
A	
B	
C	
D <i>Non-inverting input</i>	
E <i>Inverting input</i>	
F <i>Output</i>	
Which LED is lit?	

Test Point	Voltage
A	
B	
C	
D <i>Non-inverting input</i>	
E <i>Inverting input</i>	
F <i>Output</i>	
Which LED is lit?	


Test Point	Voltage
A	
B	
C	
D <i>Non-inverting input</i>	
E <i>Inverting input</i>	
F <i>Output</i>	
Which LED is lit?	

Describe what you notice when voltage D (non-inverting input) is greater than voltage E (inverting input):

Describe what you notice when voltage E (inverting input) is greater than voltage D (non-inverting input):

Circuit no.7: Adding an LDR to a comparator circuit

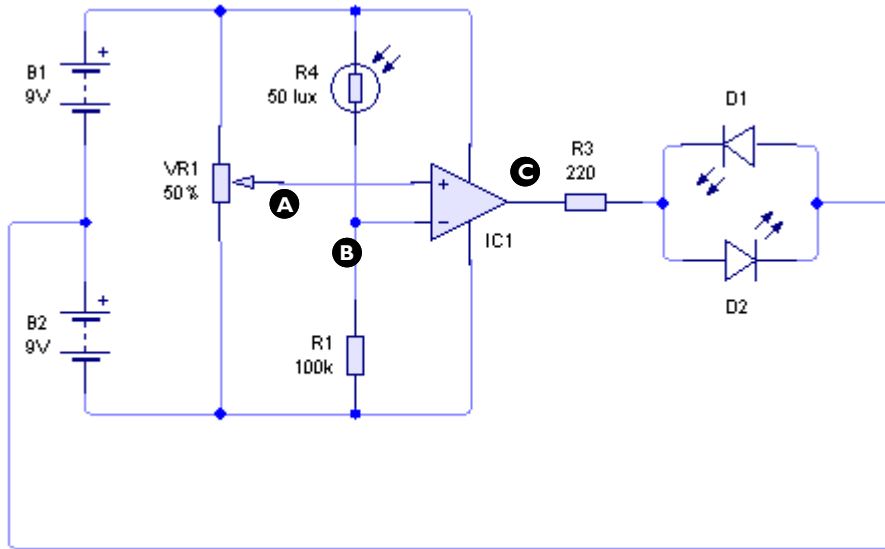Modify your circuit to include an LDR as shown below. Set the potentiometer to the 50% position. Measure the voltage at each point



Set LDR to maximum brightness

Set the LDR to minimum brightness


Test Point	Voltage
A <i>Non-inverting input</i>	
B <i>Inverting input</i>	
C <i>Output</i>	
<i>Which LED is lit?</i>	

Test Point	Voltage
A <i>Non-inverting input</i>	
B <i>Inverting input</i>	
C <i>Output</i>	
<i>Which LED is lit?</i>	

When the LDR brightness is set to maximum what is its resistance? _____

When the LDR brightness is set to minimum what is its resistance? _____

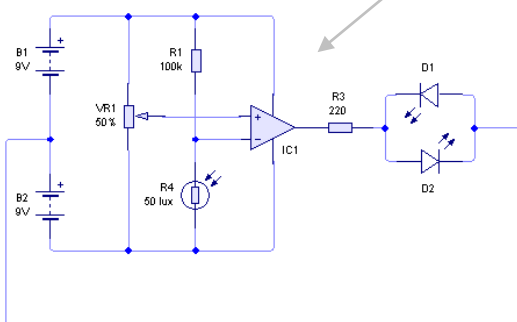
Now swap the position of the LDR and R1 as shown below and describe what you notice:



Describe what you could do to your original circuit to make it work like the circuit shown to the left and why:

Circuit no.7: Adding an LDR to a comparator circuit

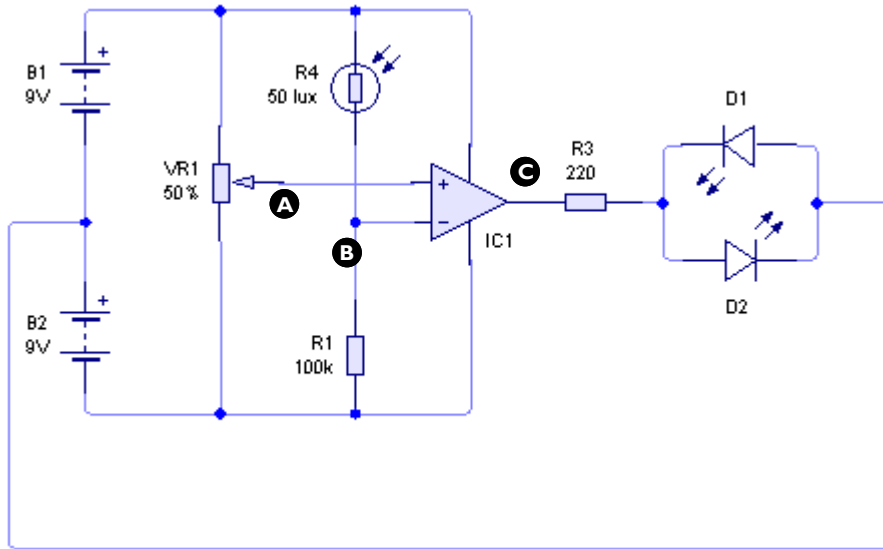Modify your circuit to include an LDR as shown below. Set the potentiometer to the **50% position**. Measure the voltage at each point



Set LDR to maximum brightness

Set the LDR to minimum brightness


Test Point	Voltage
A <i>Non-inverting input</i>	
B <i>Inverting input</i>	
C <i>Output</i>	
<i>Which LED is lit?</i>	

Test Point	Voltage
A <i>Non-inverting input</i>	
B <i>Inverting input</i>	
C <i>Output</i>	
<i>Which LED is lit?</i>	

When the LDR brightness is set to maximum what is its resistance? _____

When the LDR brightness is set to minimum what is its resistance? _____

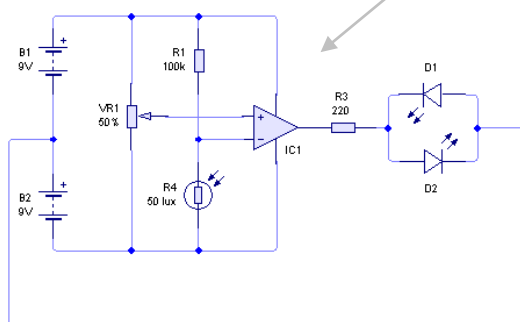Now swap the position of the LDR and R1 as shown below and describe what you notice:



Describe what you could do to your original circuit to make it work like the circuit shown to the left and why:
