

Name : _____

Target grade: _____



Design & Technology Department

GCSE Electronic Products Revision Exercises *Part 2*

Topics:

Logic Gates
4026 7-Segment Counter
4017 Decade Counter

Mr. Clarvis

Feedback sheet

Name: _____

Group: _____

Date:

Target:

Grade:

Effort:

Strengths:

Areas for development:


General comments:

Learning Objectives

- Understand that logic is used when circuits require more than one input;
- Use the following logic gates and construct their truth tables: AND, OR and NOT;
- Understand that logic gates respond to, and output, digital signals and distinguish these from analogue signals.


Task 1: Draw the symbols for the logic gates below, and draw their truth-tables, label the inputs and outputs.

AND GATE

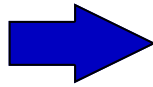


Input A	Input B	Output (Q)

OR GATE

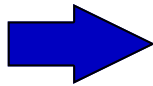

Input A	Input B	Output (Q)

NOT GATE

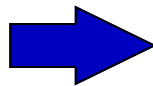

Input A	Input B	Output (Q)

Task 2: Describe the differences between analogue and digital signals.

Task 3: Complete the graphs showing a digital and an analogue signal.



Analogue Signal



Digital Signal


Task 4: Which other words can be used to describe the terms LOGIC 1 and LOGIC 0 when in relation to digital circuits?

Task 5: Describe what is meant by: PULL UP resistors and PULL DOWN resistors in relation to digital circuits and switches.


PULL UP: _____

PULL DOWN: _____

Task 6: In the space below show how a PTM switch can be used with a PULL UP resistor to put a logic 0 on the input of a NOT gate when the switch is pressed.

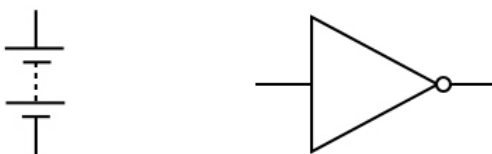

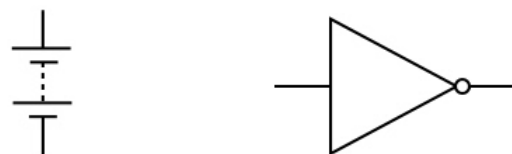Task 7: In the space below show how a PTM switch can be used with a PULL DOWN resistor to put a logic 1 on the input of a NOT gate when the switch is pressed.




Learning Objectives

- Describe what is meant by a Dual In Line (DIL) IC package;
- Identify the pin numbers on a dual in line IC;
- Describe the use of an IC socket;
- Show awareness of dedicated ICs found in toys




Task 8: What does DIL stand for? _____

Task 9: label pins on the chip shown below. Show the **two** methods used to help you identify pin number 1.

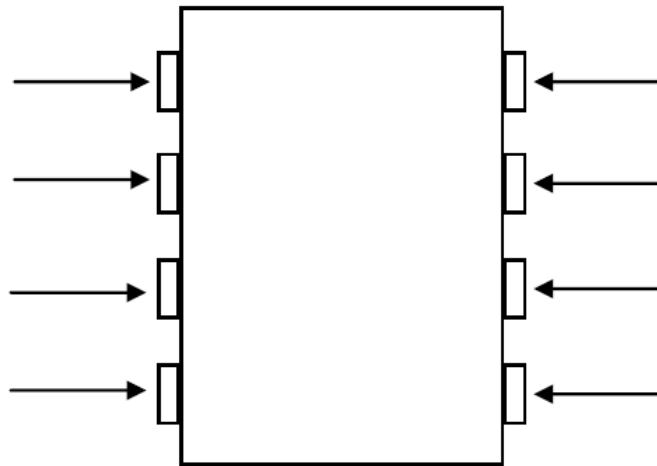

Task 10: Explain two reasons why we use a DIL socket rather than just soldering an IC straight onto a PCB (circuit board):

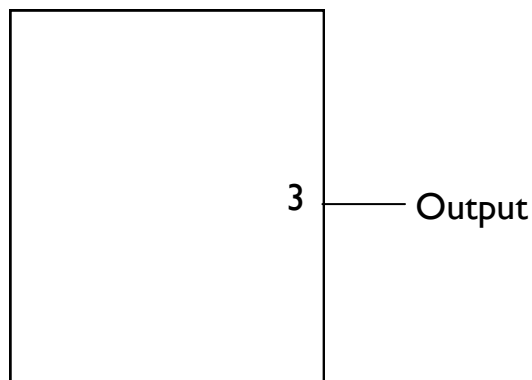Task 11: Complete the circuit symbol of a 555 timer IC.




Learning Objectives


- Be able to use 4017 decade counter
- Be able to use 4026 7-segment counter



Task 12: Shade the images below to show how the digits 0 to 9 are displayed on an LED display.

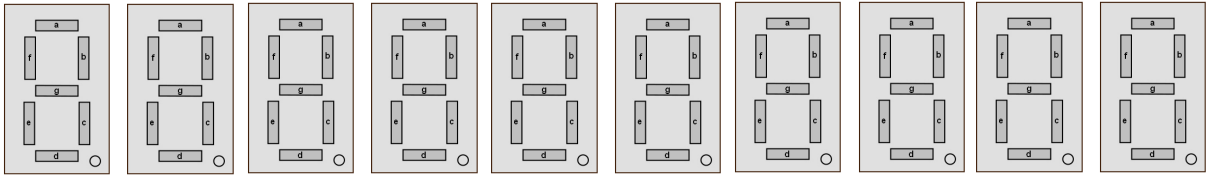

Task 13: Draw the circuit diagram of a 4026 7-segment counter including two switches—one to increase the count value and one to reset the counter.

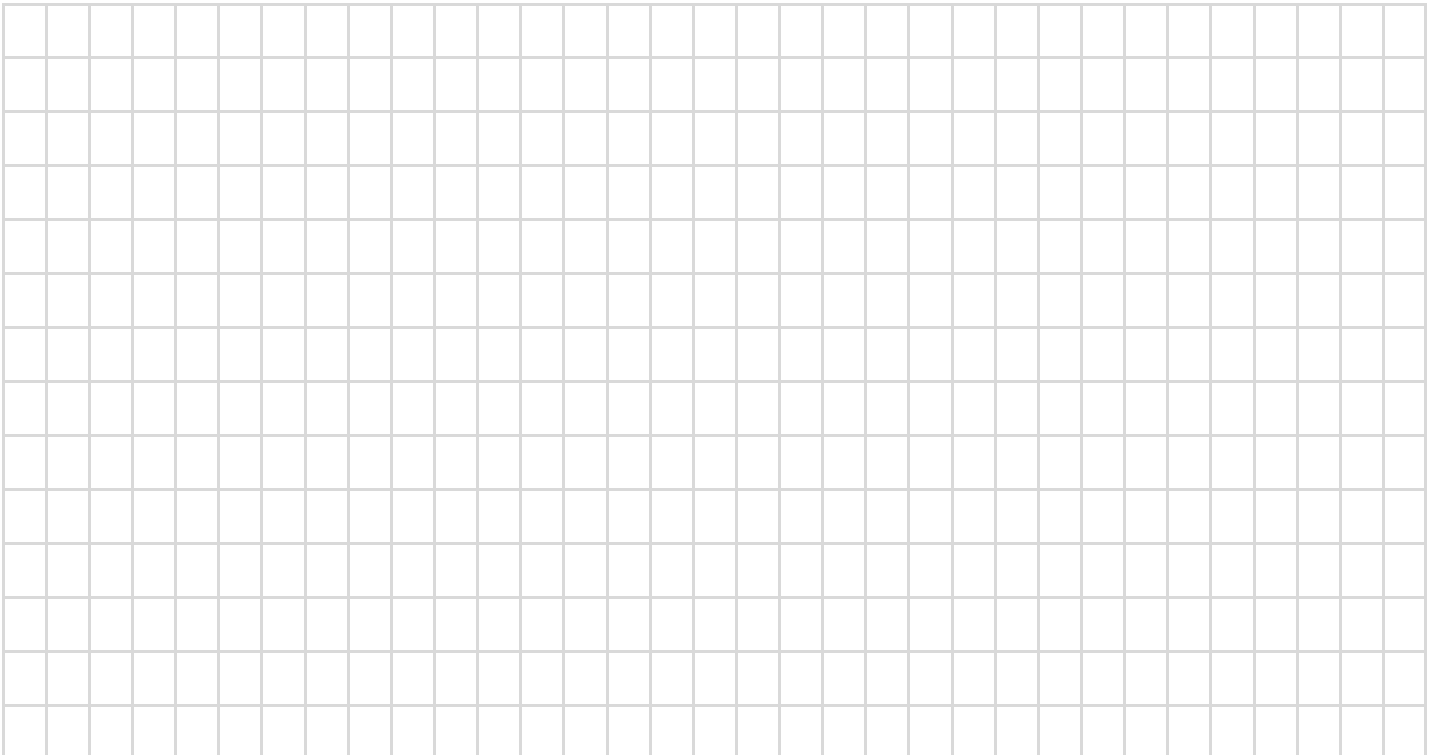

Task 14: Explain the function of the following input and output pins on a 4026 counter.

CE: _____


EO: _____

R: _____


“<” symbol: _____

Learning Objectives

- Be able to use 4017 decade counter
- Be able to use 4026 7-segment counter

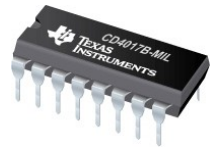

Task 15: Draw the circuit diagram of a 4017 decade counter including two switches—one to increase the count value and one to reset the counter.

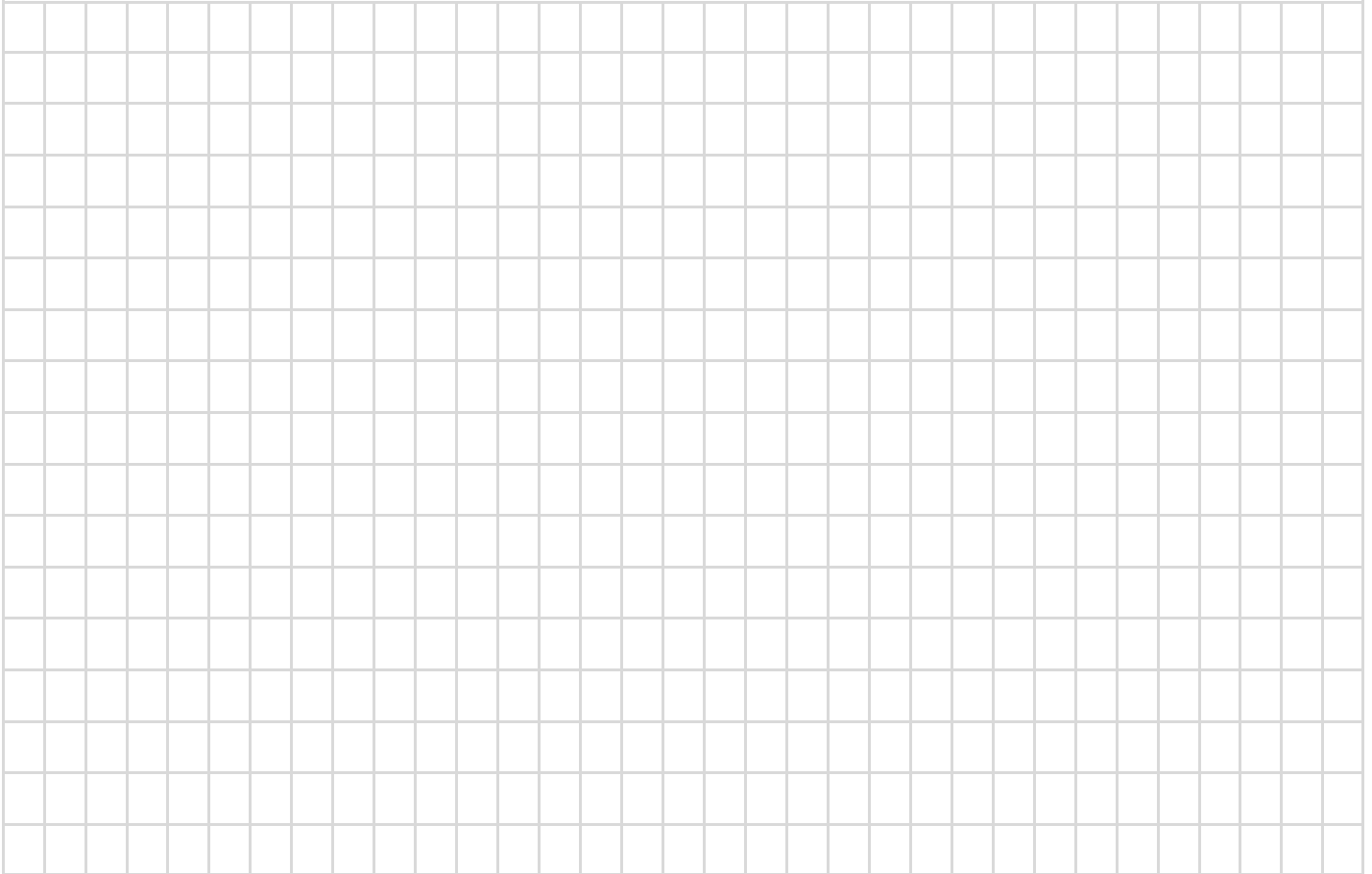

Task 16: Explain how the circuit above works.
